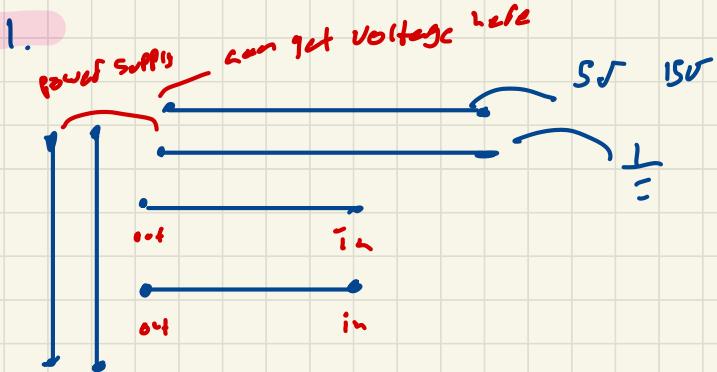


## LAB 1

In ICS lab we mainly got  
accustomed to the lab equipment  
and built some simple circuits



2. a) Fig 1  $\Rightarrow$  we measured 5 Volts across the resistor with ground connection and 0 Volts without!  
→ No reference point to measure the voltage w/o
- b) Fig 3  $\Rightarrow$  .46 milliamps in the closed circuit

c) Voltage : 5.06

$$\frac{V_1}{V_2} = \frac{5.07}{5.06}$$

$$\frac{V}{I} = \frac{5.07}{46 \times 10^{-3}} = 11021.74 \text{ ohms}$$

3) figure 5  $\Rightarrow$   $V_{Rx} = \frac{R_1}{R_1 + R_2} \times V_{in}$

$$2.5V = \frac{10k\Omega}{20k\Omega} \times 5 \text{ Volts}$$

We got 2.485  $\rightarrow$  very similar measurements


4.  $V_{Rx} = \frac{R_1}{R_1 + R_2} \times V_{in}$

' If  $R_1 \gg R_2$  then taking the limit of the equation should give

$$V_{out} = 1$$

If  $R_2 \gg R_1$ , then taking the limit that will approach  $\phi$ .

5)

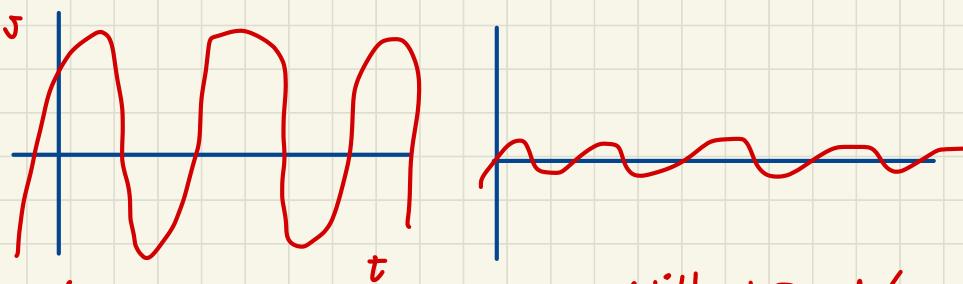

with out terminat

$$\text{Peak to Peak} = 1.96 \text{ V}$$

$$f = 1.244 \text{ kHz}$$

with terminat

$$\text{Peak to Peak} = 220 \text{ mV}$$

$$f = 2.252 \text{ kHz}$$

- much lower peak to peak voltage with the terminator due to its acting like a resistor in the circuit



- the oscilloscope seems more like a voltmeter due to it outputting sinusoidal waves of waveforms with respect to voltage as the independent variable

b)

When triggered Level is outside the range of the displayed Signal the graph makes and shows oscillation.

- trigger level inside of the Peak to Peak

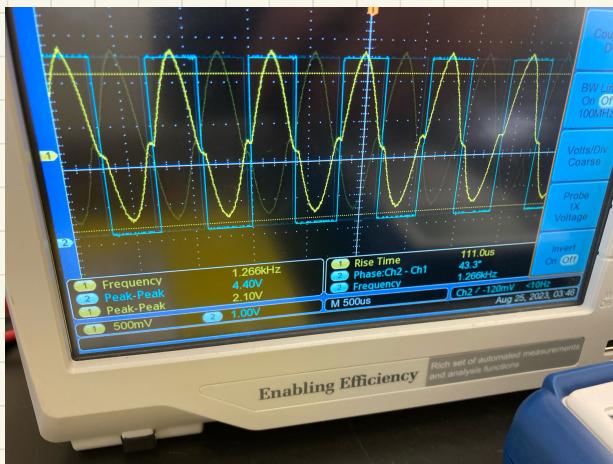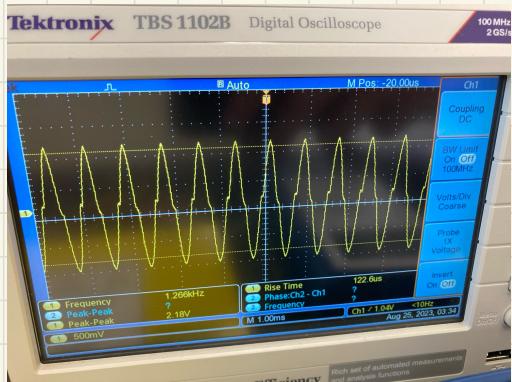Voltage range of the sin wave stops oscillations and almost freezes the function in place. Allowing for a much clearer image of the wave if the oscillation is happening fast.



7. For <sup>in</sup> DC the DC offset knob shifts the entire function vertically.

For AC trim knobs changes the amplitude.

8)

$$V_{out} = V \frac{R_L}{R_o + R_L} \quad \frac{1}{V_o} \propto \frac{1}{R_L}$$

$$\frac{1}{V_o} = \frac{1}{V} \frac{R_o + R_L}{R_L}$$

$$\frac{1}{V_o} = \frac{R_o}{V R_L} + \frac{1}{V}$$

a) 10 Hz 1 kHz 100 kHz

Slope (voltage) 1.0015 0.9855 0.025

Second 1.08 1.511 .005

Third .794 .767 .254

10) R-L time 34.41 ns

## LAB 2

In this LAB, we focused on RC circuits. We made High and Low pass filters and took measurements and did derivations accordingly.

## Lab 2

1) (a)

circuit A

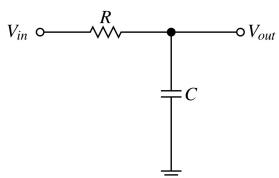


Figure 2.1: Circuit A.

$$\text{Rise time} = 400\text{ns}$$


$$\text{Fall time} = 424\text{ns}$$

$$RC = 24\text{ns}$$

measured.  $T = RC = 10^{-4}\text{ seconds}$  *computed*

$$.000024 \neq 0.0001 \text{ seconds}$$

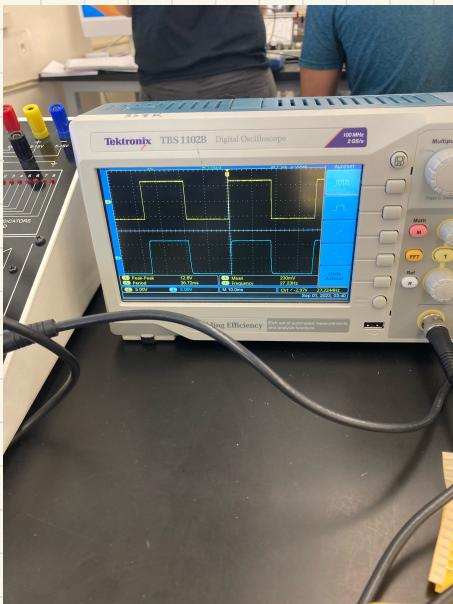a whole decimal place off but still slightly similar




1b)



2)




3)

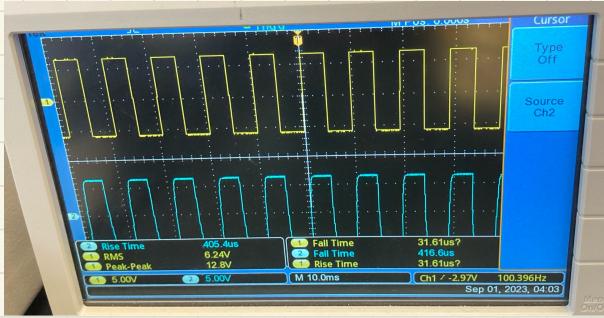



The output changes from square to its integral because the blue line is becoming more and more a triangle wave. If you plot the derivative of a triangle wave it will give a square wave.

4)

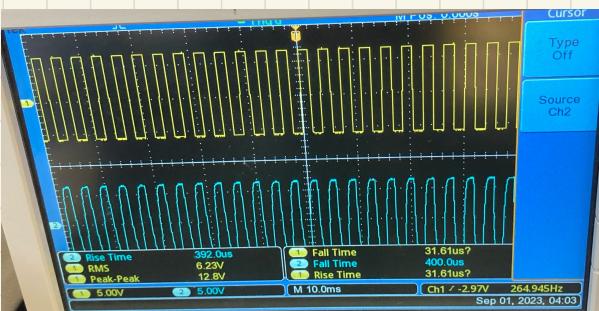

$\zeta$	$f_{oct}/f_{sin}$	$f$	$\phi$
0.68	$\cdot \frac{8.4}{12.4}$	807 Hz	$-43.6^\circ$
0.81	$\cdot \frac{10}{12.4}$	519 Hz	$-26.5^\circ$
0.92	$\cdot \frac{11.6}{12.4}$	253 Hz	$-35.7^\circ$
0.71	$\cdot \frac{8.8}{12.4}$	696 Hz	$-40.1^\circ$
0.54	$\cdot 6.8 / 12.4$	1.05 kHz	$-60.8^\circ$
0.42	$\cdot 5.2 / 12.4$	1.39 kHz	$-57.6^\circ$
0.34	$\cdot 4.7 / 12.4$	1.8 kHz	$-61.7^\circ$
0.31	$\cdot 3.8 / 12.4$	2.19 kHz	$-72.3^\circ$
0.25	$\cdot 3.2 / 12.4$	2.69 kHz	$-59^\circ$
0.16	$\cdot 2 / 12.4$	4.8 kHz	$-76.5^\circ$
0.13	$\cdot 1.6 / 12.4$	6.06 kHz	$109^\circ$
0.11	$\cdot 1.4 / 12.4$	7.4 kHz	$72^\circ$

c)

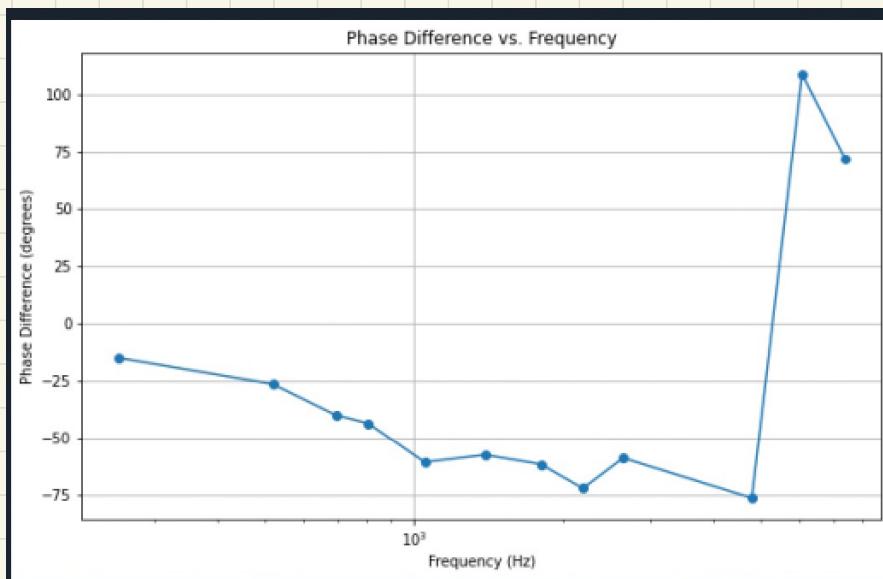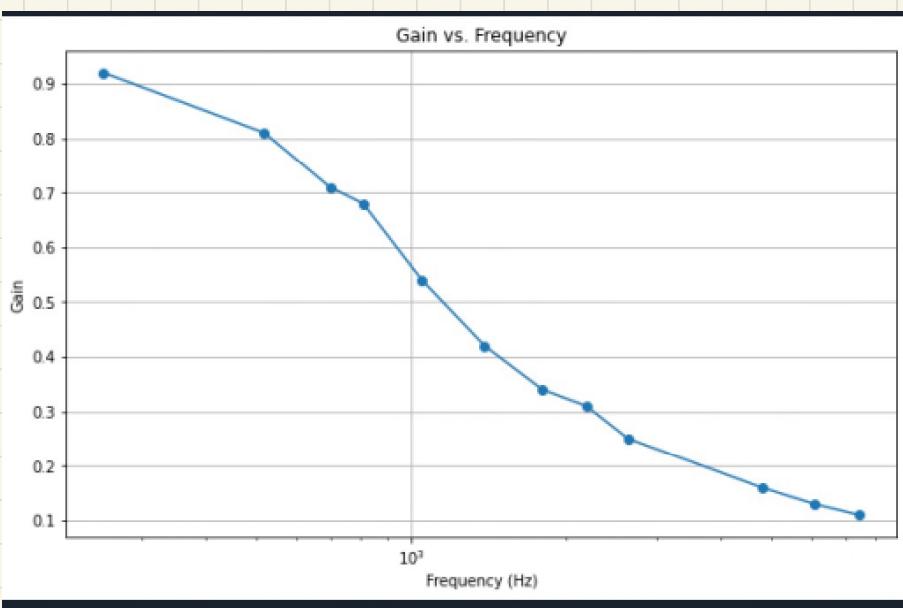

## 2. Circuit B

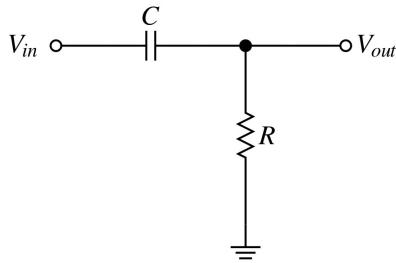


Figure 2.2: Circuit B.

15

$$R_L = 10^{14}$$


$$\text{rise ch1} = 321.4 \mu\text{s}$$

$$\text{fall ch1} = 220.4 \mu\text{s}$$


$$\text{rise ch2} = 264.3 \mu\text{s}$$

$$\text{fall ch2} = 1.17 \mu\text{s}$$


b)

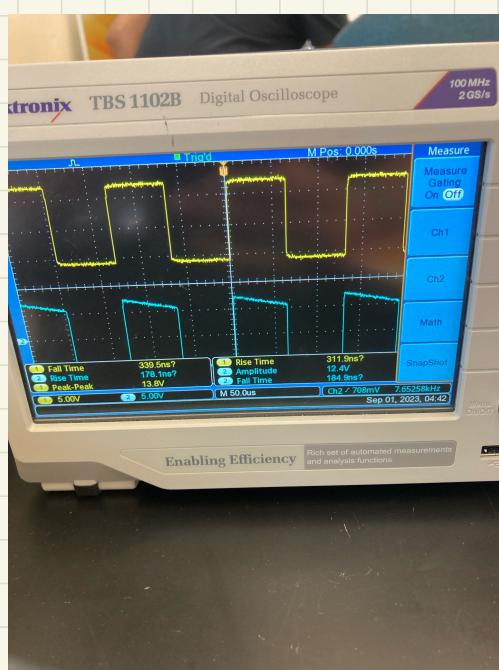


①

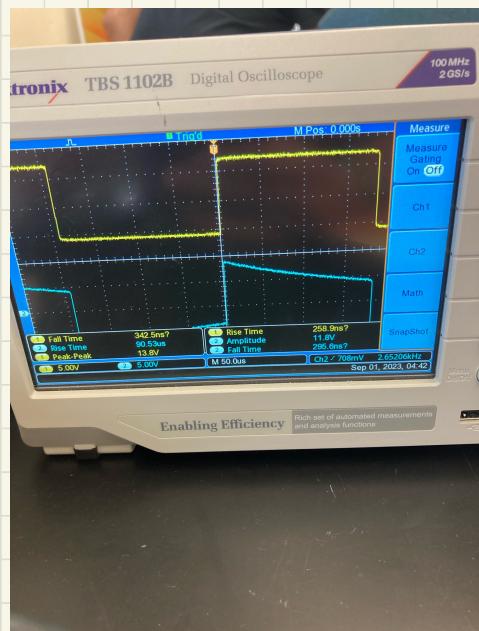

②

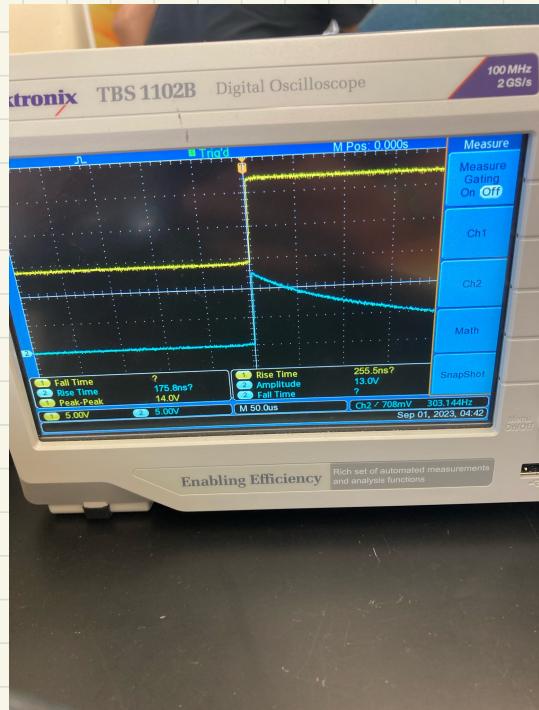

(3)

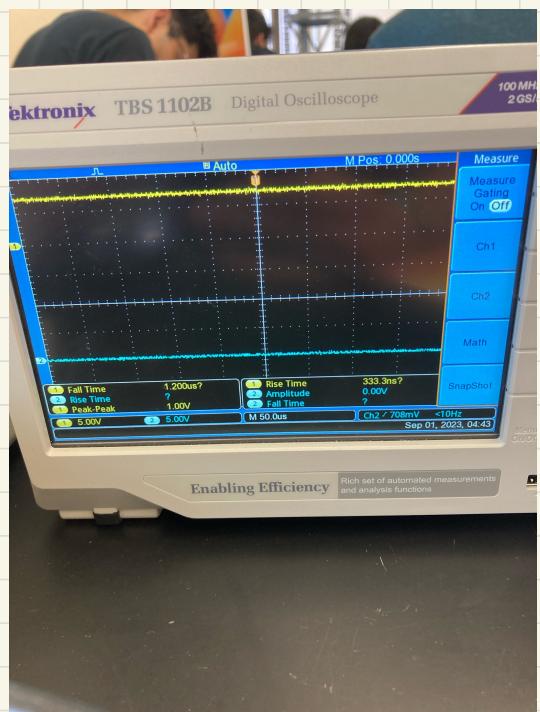

(4)

AS we decreased the frequency you  
 can tell channel 2 (the blue line)  
 behaves more like the derivative bc of the  
 spikes in the graph and the downward slope  
 after indicating a decrease in the rate of  
 change

(c)

f

$$\frac{r_{oo} +}{r_{in}}$$

 $\phi$ 

• 167.59 kHz

$$\frac{12}{11.8} \quad 1.02$$

 $-3.78^\circ$ 

• 118.5 kHz

$$\frac{12}{11.8} \quad 1.02$$

 $-3.83^\circ$ 

• 106.86 kHz

$$\frac{12}{11.8} \quad 1.07$$

 $2.35^\circ$ 

• 82.82 kHz

$$\frac{12}{11.8} \quad 1.02$$

 $-2.98^\circ$ 

• 60 kHz

$$1.5$$

 $1.45^\circ$ 

• 45 kHz

$$1$$

 $-4.05^\circ$ 

• 26.34 kHz • 98

$$11.8 / 12.2$$

 $-3.78^\circ$ 

• 21 kHz

$$\cdot 98$$

$$11.8 / 12$$

 $-4.58^\circ$ 

• 17.67 kHz

$$\cdot 98$$

$$12 / 12.2$$

 $-4.38^\circ$ 

• 14.74 kHz

$$1$$

$$12 / 12$$

 $-4.25^\circ$ 

• 10.61 kHz

$$\cdot 98$$

$$12 / 12.2$$



 $-2.93^\circ$ 

• 8.68 kHz

$$\cdot 98$$

$$12 / 12.2$$

 $-1.88^\circ$

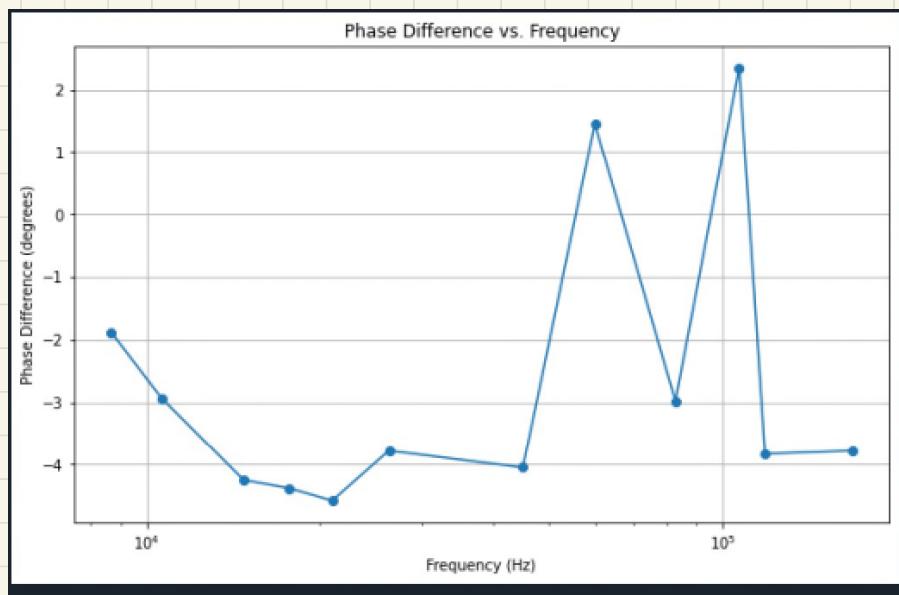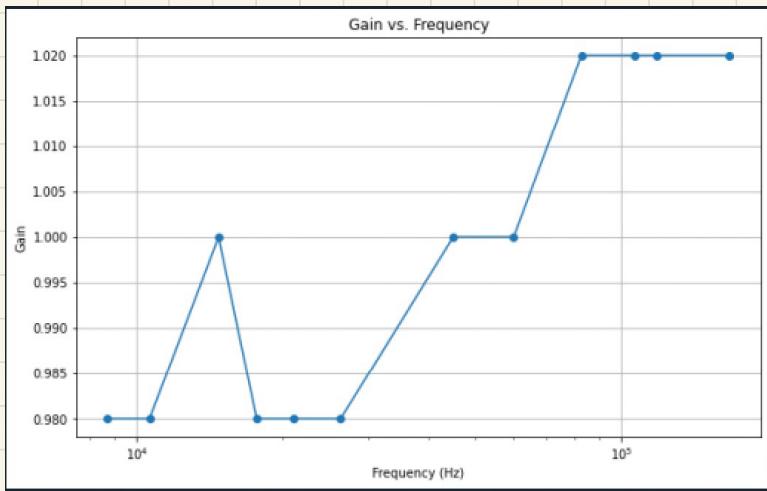

Lab 2 #3)

$$Z_{eq} = R + \frac{1}{j\omega C}$$

$$V_{out} = V_{in} \times \frac{Z_{out}}{Z_{total}}$$

$$= V_{in} \cdot \frac{R}{R + \frac{1}{j\omega C}}$$

$$\frac{V_{out}}{V_{in}} = \frac{j\omega RC}{1 + j\omega RC}$$

gain as a function  
of frequency

Phase angle

$$\frac{V_{out}}{V_{in}} = \frac{j\omega RC(1 - j\omega RC)}{(1 + j\omega RC)(1 - j\omega RC)}$$

$$= \frac{j\omega RC - (j\omega RC)^2}{1 - (j\omega RC)^2}$$

$$= j\omega RC - j^2 \omega^2 R^2 C^2$$
$$\frac{}{1 - j^2 \omega^2 R^2 C^2}$$

$$= \underbrace{\frac{\omega^2 R^2 C^2}{1 + \omega^2 R^2 C^2}}_{real} + \underbrace{\frac{j\omega RC}{1 + \omega^2 R^2 C^2}}_{imaginary}$$

$$\phi = \tan^{-1} \left( \frac{b}{a} \right)$$

continued

$$\phi = \tan^{-1} \left( \frac{\frac{wRC}{1+w^2R^2C^2}}{\frac{w^2R^2C^2}{1+w^2R^2C^2}} \right)$$

$$\phi = \tan^{-1} \left( \frac{wRC}{w^2R^2C^2} \right) = \tan^{-1} \left( \frac{1}{wLC} \right) \checkmark$$

4)

$$\frac{V_{out}}{V_{in}} = \frac{Z_{out}}{Z_{in} + j\omega L} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC} \checkmark$$

$$\phi = -\tan^{-1}(wRC) \checkmark$$

## Lab 3

In Lab 3 we built and observed passive filters. We made a 2 stage RC bandpass filter and two, LRC bandpass filters. We observed resonance frequencies and mostly measured the gain.

### Lab 3

1) 3.1 nF

$$1.939 \text{ k}\Omega = R_1$$

$$C_1 = .95_{-ff} .98 \text{ nF}$$

$$5.1 \text{ k}\Omega$$

$$9.96 \text{ k}\Omega = R_2$$


$$0.5 \text{ C } 0 \text{ M}\Omega =$$

$$C_2 = 9.67 \text{ nF}$$

Data Points

V <sub>out</sub>	V <sub>in</sub>	Frequency
0.092	98 mV	1.000 Hz
0.123	130 mV	2.000 Hz
0.136	144 mV	4.000 Hz
0.14	148 mV	7.000 Hz
0.14	146 mV	9.000 Hz
0.142	150 mV	8.400 Hz
152 mV	1.000 V	8.700 Hz

-143	152 mV	1.065	9000 Hz
-143	152 mV	1.065	1500 Hz
-144	158 mV	1.065	11000 Hz
-14	148 mV	1.06	13000 Hz
-176	144 mV	1.06	19000 Hz
-128	136 mV	1.06	30 kHz

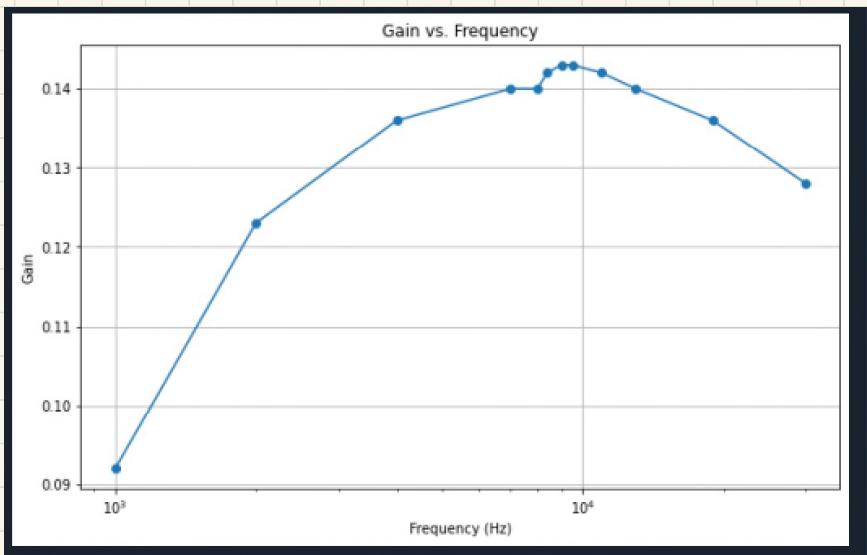

2)

$$\left( \frac{U_{\text{intermediate}}}{U_{\text{in}}} \right) = \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1} \quad \begin{matrix} \text{from Lab 2} \\ (\text{High Pass}) \end{matrix}$$

first filter

$$\frac{U_{\text{out}}}{U_{\text{intermediate}}} = \frac{1}{1 + j\omega R_2 C_2} \quad \begin{matrix} \text{from Lab 2} \\ (\text{Low Pass}) \end{matrix}$$

second filter

$$\text{total gain} = \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1} \times \frac{1}{1 + j\omega R_2 C_2}$$

- since  $R_2 \gg R_1$ , the load from the first filter will not interfere with the performance of the second filter.

3)

$$R = 218.4 \Omega$$

$$C = 470 \mu F$$

$$L = 20 \mu H$$

$$V_o = \frac{1}{\sqrt{LC}} = 0.01$$

As it says we  
 couldn't get this circuit  
 to show any data on the oscilloscope,  
 I think the circuit could be essentially  
 short circuiting due to the capacitor  
 not being charged up and then driving  
 the current.

$$\text{since } V_{in} = V_R + V_L$$

$$V_R = V_L - V_{in}$$

We can use these voltages  
 to find  $V_R$  as a function  
 of frequency by plotting

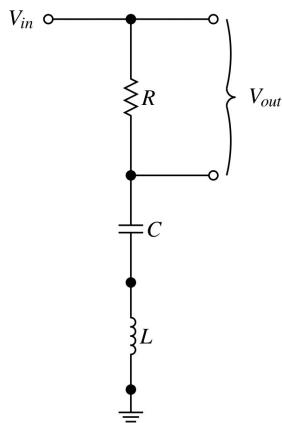


Figure 3.2: LRC Bandpass filter (Prob. 3).

4)

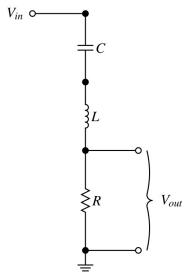


Figure 3.3: LRC Bandpass filter (Prob. 4).

Resonant frequency = 1800 kHz

$$1.8 \text{ kHz} \quad V_{in} = 10.2 \text{ V}, \quad \omega_{out} = 8.8 \text{ rad/s}$$

$$260 \text{ Hz} \quad V_{in} = 10.4 \text{ V}, \quad V_{out} = 8 \text{ V}$$

$$32.5 \text{ kHz} \quad V_{in} = 10.2 \text{ V}, \quad \omega_{out} = 7.2 \text{ rad/s}$$

$$115 \text{ kHz} \quad V_{in} = 10.2 \text{ V}, \quad \omega_{out} = 3.4 \text{ rad/s}$$




$$R_{eq} = R_1 + R_2$$

$$= 102.6 \Omega + 100.2 \Omega$$

$$C = 8.18 \mu\text{F}$$

$$L = 1 \times 10^{-3} \text{ H}$$

4 different wave forms

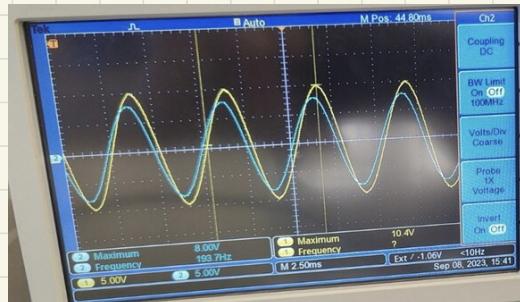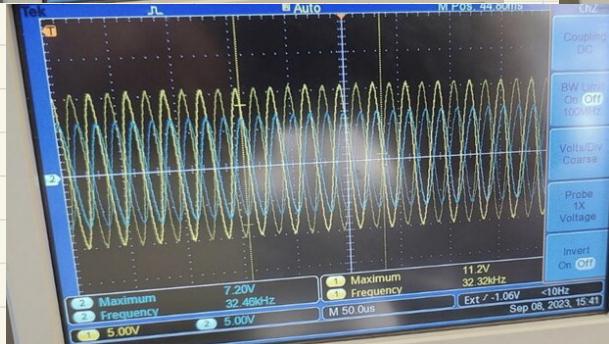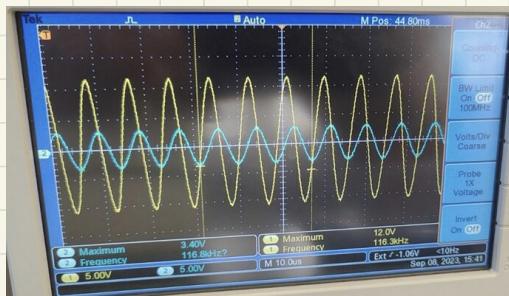

5)

$$R = 500 \Omega, 100 \Omega$$

$$L = 8.18 \mu F$$

$$C = 0.001 \text{ F}$$

$$\omega_0 = \frac{1}{2\pi\sqrt{LC}} = 1.76 \text{ kHz}$$

for both 100  $\Omega$   
and 500  $\Omega$   
resistor

- If you want sharper resonance you need higher resistance.

6)

$$L = 0.001 \text{ H}$$

$$C = 8.18 \mu F$$

$$R = 500 \Omega$$

$$\frac{Z_{out}}{Z_{in}}$$

$$Z_C = \frac{1}{j\omega C}, Z_L = j\omega L$$

$$\frac{1}{Z_{box}} = \frac{1}{Z_C} + \frac{1}{Z_L} = \frac{-\omega^2 L C + 1}{j\omega C}$$

$$Z_{box} = -j\omega C / 1 - \omega^2 LC$$

$$Z_{\text{total}} = R + \frac{-j\omega L}{1 - \omega^2 LC}$$

$$\frac{V_{out}}{V_{in}} = \frac{Z_{out}}{Z_{total}} = \frac{-j\omega L / (1 - \omega^2 LC)}{R - j\omega L / (1 - \omega^2 LC)}$$

$$= \frac{-j\omega C}{R(1 - \omega^2 LC) + j\omega C}$$

$$\approx \frac{\omega L}{\omega^2 RLC - \omega L + R} \quad \checkmark$$

$$Q = \frac{(1.76 \times 10^3) \times 10^{-3}}{500 \Omega} = 3.52$$

$$\omega_s = \frac{1}{\sqrt{LC}} = 1.76 \times 10^3 \text{ rad/s}$$