

Lab Report 2: Lab 4-6

Enrique Rivera Jr
Marcus

September 30, 2024

Lab 4: Diodes

Important Concepts

- **Diode:** A semiconductor device that allows current to flow in one direction only. It has two terminals: an anode (+) and a cathode (-).
- **Voltage Divider:** A circuit used to create a voltage less than or equal to the input voltage.
- **Diode Forward Voltage Drop:** Typically around 0.7V for silicon diodes.
- **Zener Diode:** Designed to operate in reverse bias, with a specified breakdown voltage.

Equations

- **Diode Equation:**

$$I = I_s \left(e^{\frac{V}{nV_T}} - 1 \right)$$

- **Voltage Divider:**

$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$

- **Ripple Voltage:**

$$V_{ripple} = \frac{I_{load}}{fC}$$

0.1 FYR Questions

1. **Diode Identification and Voltage Drop:**

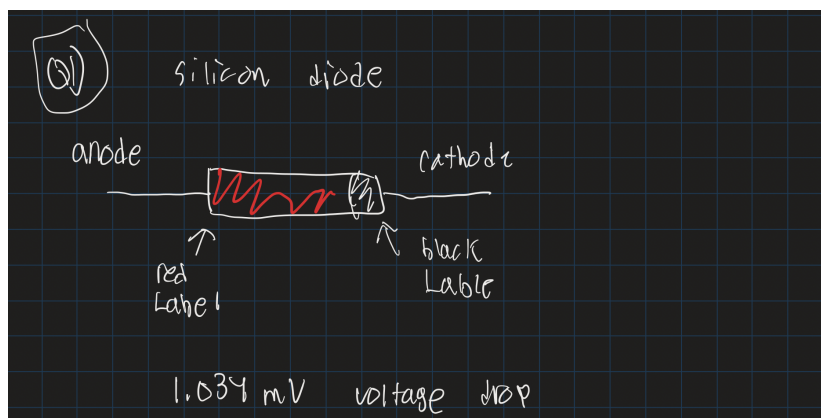


Figure 1: Drawing of Diode

2. Diode Circuits: The diode behaves like a switch; it is on when forward-biased ($V_{in} > 0.7V$), and off otherwise.

The Yellow line represents the V_{in} , the Blue line represents the V_{out} .

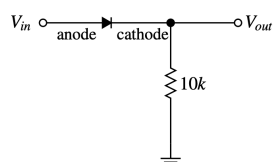


Figure 4.1: Diode Circuit 1.

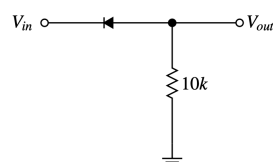


Figure 4.2: Diode Circuit 2.

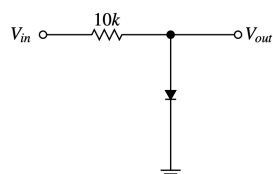


Figure 4.3: Diode Circuit 3.

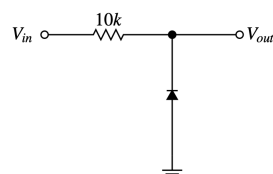


Figure 4.4: Diode Circuit 4.

Figure 2: Circuits For This Question

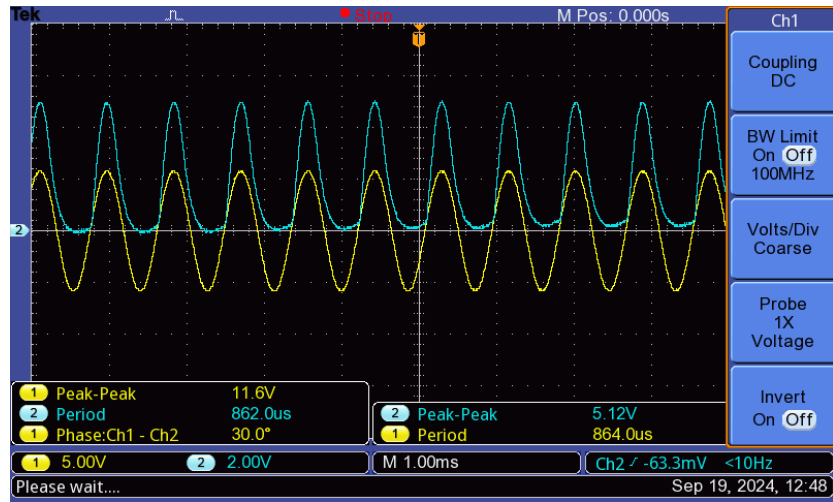


Figure 3: Circuit 1 Results

Description: A forward-biased diode in series with a resistor.

Expected Behavior: The diode will conduct (be "on") when the input voltage V_{in} is greater than the forward voltage of the diode (about 0.7V for a silicon diode). When the input drops below 0.7V, the diode will be off, and V_{out} will be near zero.

Oscilloscope Data: In the graph, you can see that the yellow waveform (V_{in}) is sinusoidal, and the blue waveform (V_{out}) shows clipping at approximately 0.7V, confirming that the diode only conducts when $V_{in} > 0.7V$.

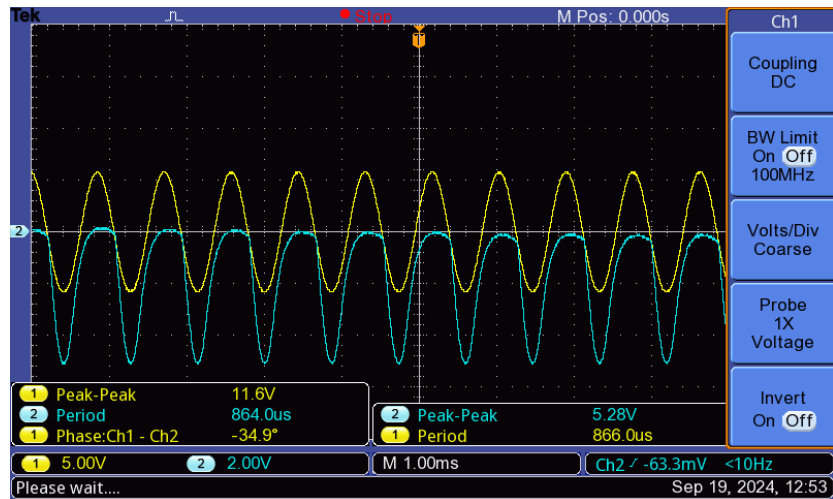


Figure 4: Circuit 2 Results

Description: A reverse-biased diode in series with a resistor.

Expected Behavior: In this case, the diode will not conduct under normal forward voltage conditions, as it is reverse-biased. Hence, V_{out} will be almost zero throughout the entire cycle of V_{in} .

Oscilloscope Data: The second graph shows that the blue waveform (V_{out}) is almost flat, indicating the diode is not conducting, as expected for a reverse-biased diode.

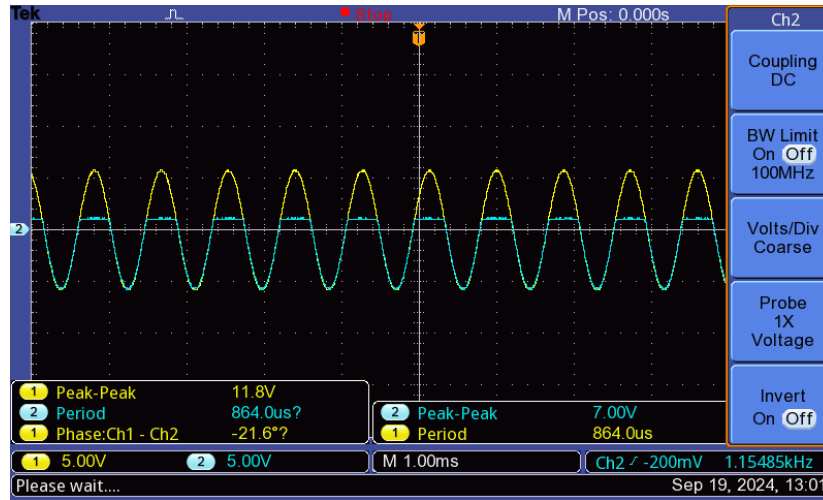


Figure 5: Circuit 3 Results

Description: A forward-biased diode, with the diode grounded.

Expected Behavior: Similar to Circuit 1, but this time, the diode is connected to the ground. The output V_{out} will be clamped at 0.7V during the positive cycle of V_{in} , and the diode will conduct when $V_{in} > 0.7V$.

Oscilloscope Data: In the third graph, the blue waveform again shows clipping at around 0.7V, indicating that the diode is conducting when $V_{in} > 0.7V$, and is off otherwise.

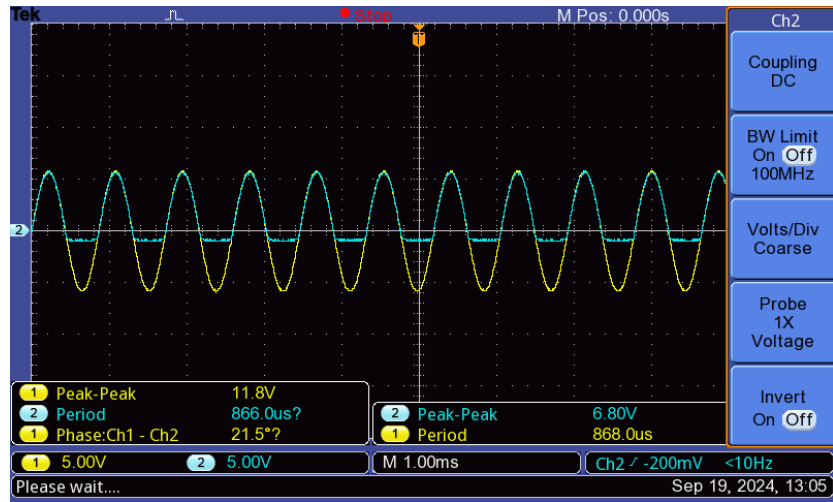


Figure 6: Circuit 4 Results

Description: A reverse-biased diode, similar to Circuit 2 but with reversed polarity.

Expected Behavior: The diode will not conduct during the positive cycles of V_{in} , but it may conduct slightly during negative cycles if the reverse breakdown voltage is reached. However, for most practical situations, the output will be near zero.

Oscilloscope Data: The fourth graph shows minimal activity on the blue waveform (V_{out}), confirming that the diode remains off, as expected for a reverse-biased diode.

3.Voltage Clamp Circuit: Adjusting the +1V shifted the output. The diode was **on** when V_{in} exceeded the forward voltage and bias.

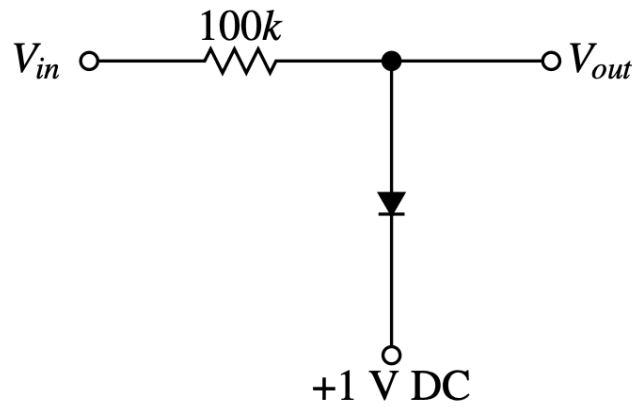


Figure 7: Circuit For Question 3

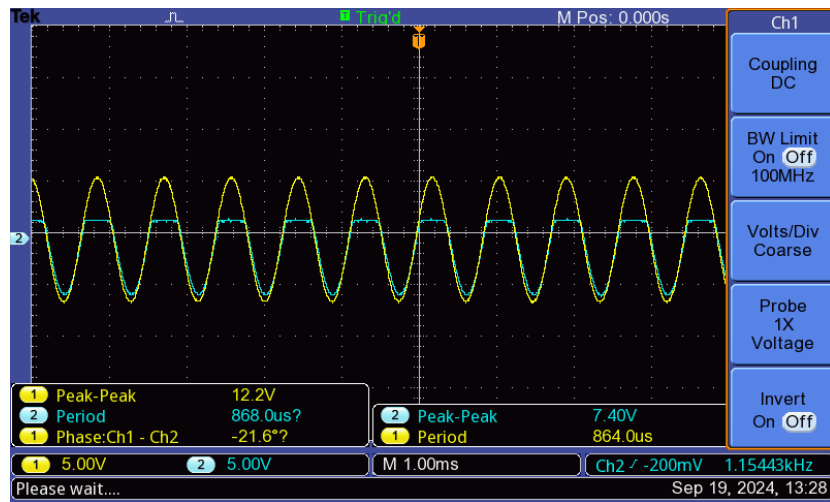


Figure 8: Circuit with +1V Shift. We can see that on V_{out} we are seeing a 1V shift will keeping the negative cycle.

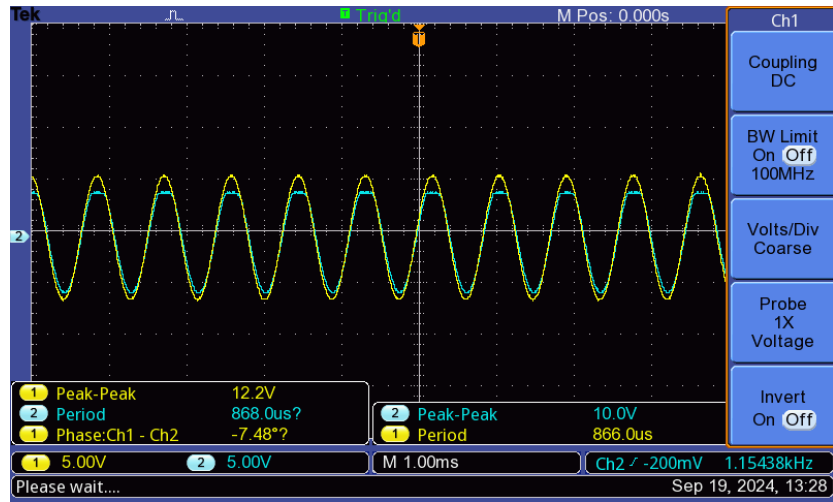


Figure 9: Circuit with 3.5V Shift. We can see that on V_{out} we are seeing a 3.5V shift will keeping the negative cycle.

4. **Two Diode Circuit** Sketched regions where D_1 and D_2 were on and off, showing rectification.

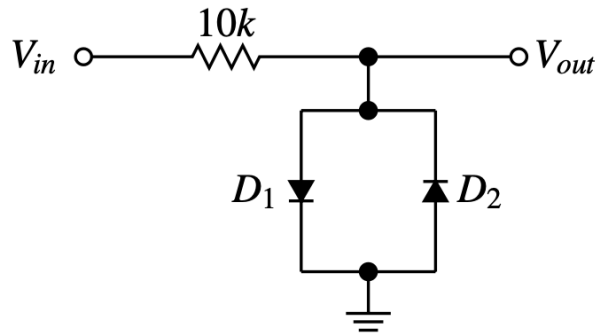


Figure 10: Circuit for Question 4

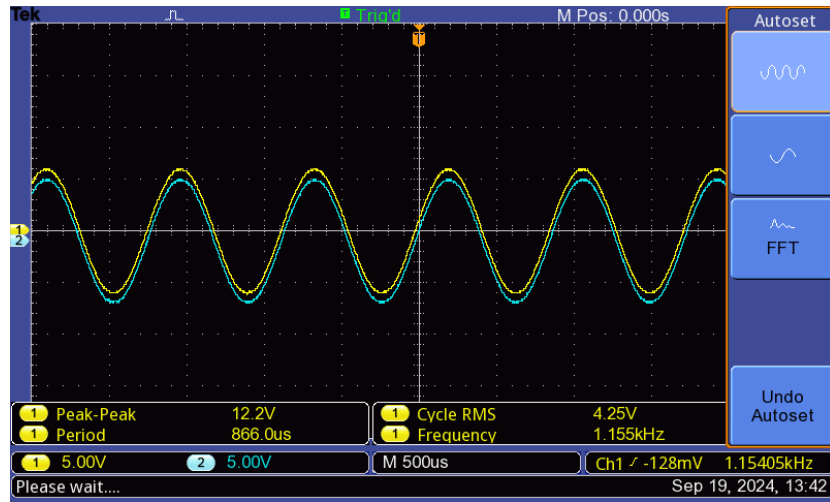


Figure 11: Circuit Results

Explanation of Diode Behavior: D1 (Forward Biased): When the input signal is positive, D1 conducts and the output voltage is clamped near 0.7V. D2 (Forward Biased): When the input signal is negative, D2 conducts and the output is clamped near -0.7V.

Regions of On and Off States: D1 is on during the positive half-cycle of the input waveform when $V_{in} \geq 0.7V$. D2 is on during the negative half-cycle of the input waveform when $V_{in} \leq -0.7V$. During these times, the output is clamped to the diode's forward voltage, limiting the maximum and minimum values of V_{out} .

5. Ripple and DC The plot of V_{DC}/V_{ripple} versus R indicated a smoother rectification with higher resistance.

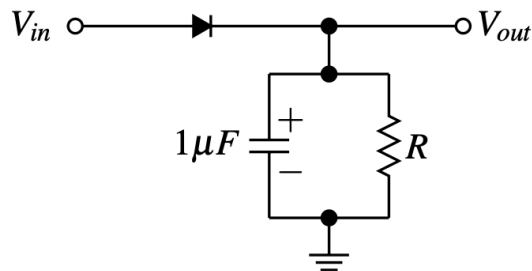


Figure 12: Circuit For Question 5

Question 5

We used a capacitor with a capacitance of $C = 0.94 \mu F$ and resistances of $R_1 = 106.4 k\Omega$ and $R_2 = 48.7 k\Omega$. The circuit was set at a frequency of 1.5 kHz.

The ripple voltage V_{ripple} is defined as:

$$V_{ripple} = V_{\max} - V_{\min}$$

The DC voltage V_{DC} is given by:

$$V_{DC} = \frac{V_{\max} + V_{\min}}{2}$$

We recorded the following values for different resistances:

Filtering Resistance (R)	V_{ripple} (V)	V_{DC} (V)
100 k Ω	0.6	4.44
50 k Ω	0.4	4.76
10 k Ω	0.2	4.86
5 k Ω	0.8	4.2
200 Ω	3.4	1.51
500 Ω	3.0	2.32

Table 1: Measured ripple voltage V_{ripple} and DC voltage V_{DC} for different filtering resistances.

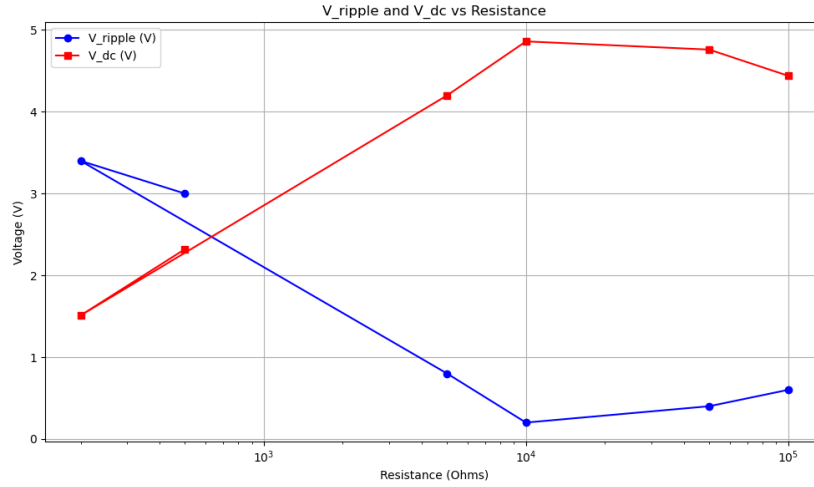


Figure 13: Graph of V_{DC}/V_{ripple} versus R

6.I-V Curve of Zener Diode: The Zener diode conducted in reverse once the 5V breakdown voltage was reached.

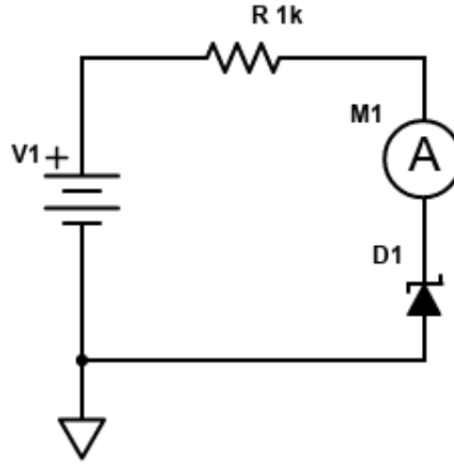


Figure 14: Graph of V_{DC}/V_{ripple} versus R

We used a Zener diode with a forward voltage of 0.702V. The resistor was set at $R = 47.6\text{ k}\Omega$. The goal was to limit the current to 50 mA.

From Ohm's law:

$$R = \frac{V}{I} = \frac{5\text{ V}}{0.05\text{ A}} = 100\ \Omega$$

Measured I-V Data: The following table presents the measured current for different voltage values across the Zener diode.

V (Volts)	I (Amperes)
1.0	2.6 mA
2.0	9.8 mA
3.0	19.6 mA
4.0	28.6 mA
5.6	36.1 mA
6.0	46.5 mA
7.0	55.6 mA
8.0	63.5 mA
9.0	73.1 mA
10.0	82.1 mA
15.0	125.1 mA
19.0	145.1 mA

Maximum Current: The maximum current measured was 145.1 mA at 19V.

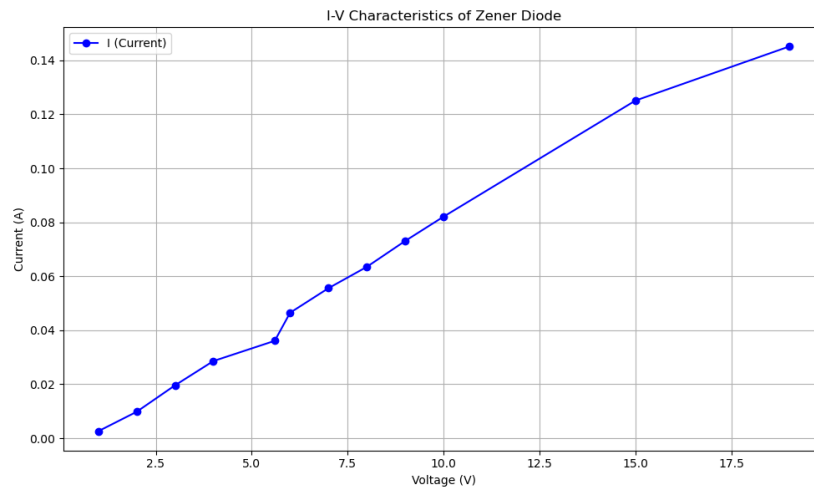


Figure 15: Graph of V_{DC}/V_{ripple} versus R